

## 108 學年度四技二專第三次聯合模擬考試 電機與電子群 專業科目(一) 詳解

108-3-03-4、108-3-04-4

1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16	17	18	19	20	21	22	23	24	25
A	D	C	B	B	A	A	B	D	C	C	B	C	D	A	C	A	D	D	C	B	D	A	B	B
26	27	28	29	30	31	32	33	34	35	36	37	38	39	40	41	42	43	44	45	46	47	48	49	50
A	C	D	C	D	A	B	C	B	B	D	A	D	C	A	C	A	B	D	C	B	A	C	D	B

### 第一部分：電子學

1. (A) 三角波的波形因數 F.F. 是 1.15
2. (D) P 型半導體呈現電中性
3. (C) 空乏區內的電場方向是由 N 側指向 P 側
4. 此電路 D<sub>1</sub> ON、D<sub>2</sub> ON

$$\text{左邊迴圈電流} \frac{10-0}{5\text{ k}} = 2\text{ mA}$$

$$\text{右邊迴圈電流} \frac{0-(-10)}{10\text{ k}} = 1\text{ mA}$$

$$\therefore I = 2\text{ m} - 1\text{ m} = 1\text{ mA}$$

5.  $V_{1m} = 110\sqrt{2}\text{ V}$ ,  $V_{2m} = 55\sqrt{2} = 77.8\text{ V}$   
半波倍壓電路,  $V_{AC} = 3V_{2m} = 3 \times 77.8 = 233\text{ V}$

6. 波形輸出平均值  $V_{o(av)} = \frac{103+97}{2} = 100\text{ V}$

$$\text{漣波最大值 } V_{r(m)} = 3\text{ V}$$

$$\text{漣波有效值 } V_{r(rms)} = \frac{3}{\sqrt{3}} = \sqrt{3}\text{ V}$$

$$\text{漣波因數百分比 } r\% = \frac{V_{r(rms)}}{V_{o(av)}} \times 100\% = \frac{\sqrt{3}}{100} \times 100\% = \sqrt{3}\%$$

7. (A)  $\alpha = \frac{\beta}{\beta+1}$

8. B、E 接面為順向偏壓；B、C 接面為逆向偏壓，故電晶體工作於主動放大區

9.  $I_C = \beta I_B$  不變,  $R_C \downarrow$ ,  $V_{CE} = V_{CC} - I_C(R_C + R_E)$  變大故工作點往 D 點移動

10. 電晶體飽和,  $V_{CE(sat)} = -0.2\text{ V}$ , 即  $V_{EC(sat)} = 0.2\text{ V}$

$$V_o = V_{CC} - V_{EC(sat)} = 10 - 0.2 = 9.8\text{ V}$$

11.  $R_{is} \cong 4\text{ k} + (300\text{ k} // 1\text{ k}) \cong 5\text{ k}\Omega$


12.  $I_E = \frac{0 - V_{BE} - (-V_{EE})}{R_E} = \frac{10}{10\text{ k}} = 1\text{ mA}$

$$r_e = \frac{V_T}{I_E} = \frac{25\text{ m}}{1\text{ m}} = 25\Omega$$

$$A_v = \frac{V_o}{V_i} = \frac{-i_c R_C}{-i_e r_e} \cong \frac{R_C}{r_e} = \frac{5\text{ k}}{25} = 200$$

$$V_{o(p-p)} = V_{i(p-p)} \times A_v = 0.4\text{ V}$$

13.

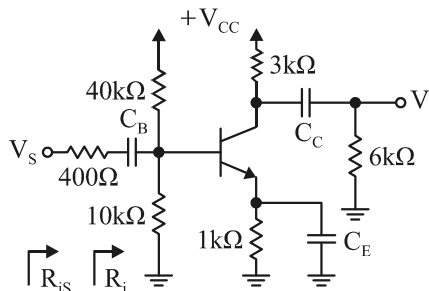

$$R_i = (40\text{ k} // 10\text{ k} // 2\text{ k}) = 1.6\text{ k}\Omega$$

$$R_{is} = 0.4\text{ k}\Omega + 1.6\text{ k}\Omega$$

$$A_{vs} = \frac{V_o}{V_s} = \frac{V_{ib}}{V_s} \times \frac{V_o}{V_{ib}} = \frac{1.6\text{ k}}{0.4\text{ k} + 1.6\text{ k}} \times \frac{-i_c \times (3\text{ k} // 6\text{ k})}{i_b r_{\pi}} = \frac{1.6}{2} \times (-250) = -200$$

14.  $Z_o = R_E // \left( \frac{i_{b2} r_{\pi 2} + i_{b1} r_{\pi 1}}{i_{e2}} \right) = R_E // \left( r_{e2} + \frac{r_{e1}}{1 + \beta_2} \right) \cong r_{e2} + \frac{r_{e1}}{\beta_2}$

15. CE: Q<sub>2</sub>, CC: Q<sub>1</sub>、Q<sub>3</sub>、Q<sub>4</sub>、Q<sub>5</sub>

16. 第二級增益 20 dBm = 10 log  $\frac{P_o}{1\text{ mW}}$   $\therefore P_o = 100\text{ mW}$

$$P_o = \frac{V_o^2}{R}, V_o = \sqrt{P_o \times R} = \sqrt{100} = 10\text{ V}$$

$$\text{第一級電壓增益為 } 20\text{ dB} = 20 \log \frac{V_x}{V_i} = 20 \log \frac{0.1}{V_i}$$

$$\therefore V_i = 0.01\text{ V}$$

$$A_{vT} = \frac{V_o}{V_i} = \frac{10}{0.01} = 1000$$

$$A_{vT(\text{dB})} = 20 \log A_{vT} = 60\text{ dB}$$

17. (A) P 通道 JFET:  $V_{GS(P)} = 3.5\text{ V}$

$$\text{夾止飽和條件: } V_{GS} < V_{GS(P)}, V_{GD} > V_{GS(P)}$$

- (B) N 通道 JFET:  $V_{GS(P)} = -3.5\text{ V}$

$$\text{夾止飽和條件: } V_{GS} > V_{GS(P)}, V_{GD} < V_{GS(P)}$$

- (C) N 通道空乏型 MOSFET:  $V_{GS(P)} = -3.5\text{ V}$

$$\text{夾止飽和條件: } V_{GS} > V_{GS(P)}, V_{GD} < V_{GS(P)}$$

- (D) P 通道空乏型 MOSFET:  $V_{GS(P)} = 3.5\text{ V}$

$$\text{夾止飽和條件: } V_{GS} < V_{GS(P)}, V_{GD} > V_{GS(P)}$$

18.  $I_D = I_{DSS} \left( 1 - \frac{V_{GS}}{V_{GS(P)}} \right)^2 = 12\text{ m} \left( 1 - \frac{-2}{-4} \right)^2 = 3\text{ mA}$

N 通道 JFET：夾止飽和條件： $V_{GD} < V_{GS(P)}$

$\therefore V_D > 2V$

$V_{DD} = I_D R_D + V_D = 3\text{ m} \times 1.5\text{ k} + V_D \quad \therefore V_{DD} > 6.5\text{ V}$

19. 電晶體特性均相同

所以  $V_{DS1} = V_{DS2} = V_{DS3} = 4\text{ V} = V_{GS1} = V_{GS2} = V_{GS3}$

$I_D = I_{D3} = K(V_{GS3} - V_T)^2 = 0.3\text{ m} \times (4 - 1)^2 = 2.7\text{ mA}$

20.  $V_D = V_{DD} - I_D R_D = 10 - 1\text{ k} \times I_D$  ,  $V_S = I_D R_S = 1\text{ k} \times I_D$

$V_{DS} = V_{GS} = 10 - 2\text{ k} \times I_D$

$I_D = k(V_{GS} - V_T)^2 = 0.75\text{ m}(10 - 2\text{ k} \times I_D - 2)^2$

$I_D = 3\text{ mA}$  ,  $V_{GS} = 4\text{ V}$  ,  $g_m = 2\text{ k}(V_{GS} - V_T) = 3\text{ mS}$

21. 
$$\frac{A_{V1}}{A_{V2}} = \frac{\frac{2\text{ m} \times 4.5\text{ k}}{1 + 2\text{ m} \times 0.5\text{ k}}}{\frac{2\text{ m} \times 4.5\text{ k}}{1 + 2\text{ m} \times (0.5\text{ k} + 1.5\text{ k})}} = \frac{5}{2}$$

22.  $V_{GS} = 0 - I_D R_S = -2\text{ V}$

$g_m = \frac{-2I_{DSS}}{V_{GS(P)}} \left(1 - \frac{V_{GS}}{V_{GS(P)}}\right) = \frac{-16\text{ m}}{-4} \times \left(1 - \frac{-2}{-4}\right) = 2\text{ mS}$

$A_v = \frac{V_o}{V_i} = \frac{-g_m R_D}{1 + g_m R_S} = \frac{-8}{1 + 2} = \frac{-8}{3}$

$Z_i = R_G = 1\text{ M}\Omega$  ,  $Z_o = R_D = 4\text{ k}\Omega$

$A_i = -A_v \times \frac{R_i}{R_o} = \frac{8}{3} \times \frac{1\text{ M}}{4\text{ k}} = \frac{2000}{3}$

23. 一周波形內於(0°~30°、150°~360°)時  $V_i < 5\text{ V}$  , 輸出高態電壓

工作週期  $\frac{(30^\circ - 0^\circ) + (360^\circ - 150^\circ)}{360^\circ} = \frac{240^\circ}{360^\circ} = \frac{2}{3}$

24. 隨耦電路  $A_v = 1$  ,  $A_{v(\text{dB})} = 20 \log 1 = 0\text{ dB}$

25.  $A_v = \left(1 + \frac{63\text{ k}}{4.5\text{ k}}\right) = 15$  , 臨界電壓  $V_+ = \frac{V_o}{A_v} = \frac{5}{15} = \frac{1}{3}\text{ V}$

$\frac{1}{3} = 0.5 \times \frac{R_x}{15\text{ k} + R_x}$  ,  $R_x = 30\text{ k}\Omega$

**第二部分：基本電學**

26. 電子往低電位移動需做功

$W = QV = |(6.25 \times 10^{17} \times 1.6 \times 10^{-19})| \times |(50 - 40)| = 0.1 \times 10 = 1\text{ J}$

27. 系統總輸出：2000 - 880 = 1120 W

系統總效率：

$\eta = \frac{P_o}{P_i} = \frac{1120}{2000} = 0.56 = \eta_A \times \eta_B = 0.8 \times \eta_B$

$\therefore \eta_B = 0.7 = 70\%$

28. 材料電阻係數  $\rho = \frac{1.724 \times 10^{-8}}{0.1724} = 10^{-7}\ \Omega\text{-m}$

$R = \rho \frac{\ell}{A} = 10^{-7} \times \frac{100}{2 \times 10^{-6}} = 5\ \Omega$


29. 總電阻： $R_T = 25 + 100 + 25 = 150\ \Omega$

總電流： $I = \frac{V}{R_T} = \frac{10}{150} = \frac{1}{15}\text{ A}$

負載電阻： $R_L = \frac{V}{I} = \frac{4}{\frac{1}{15}} = 60\ \Omega$

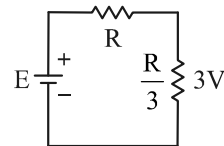30.  $I = \frac{3}{\frac{R}{3}} = \frac{9}{R}$

$E = \frac{9}{R} \times \left(R + \frac{R}{3}\right) = \frac{9}{R} \times \frac{4R}{3} = 12\text{ V}$



31. 利用重疊定理，流過 5V 電壓源電流為

$2 + 1 = 3\text{ A}$  , 故提供  $P = IV = 15\text{ W}$

5Ω 電阻兩端電壓 5V , 故消耗功率  $P = \frac{V^2}{R} = 5\text{ W}$

2A 電流源兩端電壓 5V , 故消耗  $P = IV = 10\text{ W}$

32.  $I = \frac{V}{R} = \frac{10}{5} = 2\text{ A}$

$P = I^2 R_p$  ,  $R_p = \frac{P}{I^2} = \frac{8}{2^2} = 2\ \Omega$

$E = I \times R_T = 2 \times (5 + 1 + 2) = 16\text{ V}$


33. 利用戴維寧等效電路轉換為諾頓等效電路計算

諾頓等效電阻  $R_N = 10\ \Omega$

戴維寧等效電壓  $E_{TH} = 4 \times 10 + 10 = 50\text{ V}$

諾頓等效電流  $I_N = \frac{E_{TH}}{R_N} = 5\text{ A}$

34.

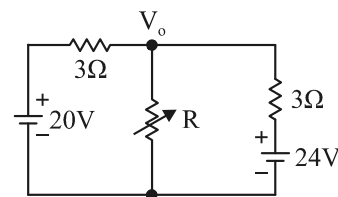

欲使 20V 電池輸出電壓則  $V_o$  電壓應小於 20V。利用節點電壓法列出克希荷夫電流方程式

$\frac{20 - V_o}{3} = \frac{V_o}{R} + \frac{V_o - 24}{3}$  ,  $R(20 - V_o) = 3V_o + R(V_o - 24)$

$44R = (3 + 2R)V_o$  ,  $V_o = \frac{44R}{3 + 2R} < 20$

$4R < 60 \quad \therefore R < 15\ \Omega$

35.  $V_b = -18\text{ V}$  , 利用節點電壓法求  $V_a$

$4 + \frac{-18 - V_a}{12} = \frac{V_a - 12}{6}$  ,  $V_a = 18\text{ V}$

$V_b = -18\text{ V}$  ,  $V_c = -18 + 24 = 6\text{ V}$


$\therefore 4\text{ A}$  電流源兩端電位差  $V_{ac} = 18 - 6 = 12\text{ V}$

故  $P = IV = 4 \times 12 = 48\text{ W}$

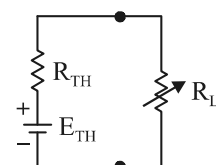36.  $R_{TH} = 2\ \Omega$  ,  $E_{TH} = 5 \times 2 + 10 = 20\text{ V}$

當  $R_L = R_{TH} = 2\ \Omega$  時

有最大功率  $P_{MAX} = I^2 R = 5^2 \times 2 = 50\text{ W}$



37. 開關閉合後  $Q_T = 20 \mu - 10 \mu = 10 \mu C$  ,  $V_1$  極性為下正上負, 當  $V_1 = V_2$  時電荷不再移動, 故  $C_1$  與  $C_2$  為並聯,  $C_T = 5 \mu + 5 \mu = 10 \mu F$  ,  $V = \frac{Q}{C} = \frac{10 \mu}{10 \mu} = 1 V$

$$V_1 = -1 V$$

38.  $E_1 = E_2$  ,  $K \frac{4 \times 10^{-6}}{r^2} = K \frac{1.6 \times 10^{-5}}{(15-r)^2}$

$$\frac{1}{r^2} = \frac{4}{(15-r)^2} , r = 5 m$$


39. (A) 特斯拉(Tesla)為磁通密度 M.K.S.制單位  
(B) 1 韋伯(Wb) =  $10^8$  馬克斯威(Maxwell)  
(D) 欲了解帶電導體在磁場中運動的受力方向可利用弗萊銘左手定則

40. 電路為並聯互消

$$L_T = \frac{L_1 \times L_2 - M^2}{L_1 + L_2 + 2M} = \frac{4 \times 6 - 1}{4 + 6 + 2} = \frac{23}{12} H$$

41. 電路趨於穩定後,  $V_{C1} = V_{C2} = E$  ,  $\frac{V_{C1}}{V_{C2}} = 1$

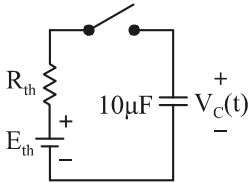42. 開關未閉合, 電路趨於穩定後電容兩端充滿 15 V 電壓, 開關閉合, 戴維寧等效電路如下圖所示



$$R_{th} = 1 k // 1 k = 0.5 k \Omega$$

$$E_{th} = \frac{E_1 R_2 + E_2 R_1}{R_1 + R_2} = \frac{40 k}{2 k} = 20 V$$

$$\tau = RC = 0.5 k \times 10 \mu = 5 m(sec)$$

電容器兩端電壓為 15 V 加上 5 V 電動勢對電容器充電

$$V_C(t) = 15 + 5(1 - e^{-\frac{10 m}{5 m}}) = 20 - 5e^{-2}$$


43.  $v(t) = V_m \sin(\omega t + \theta_1)$

$$i(t) = I_m \cos(\omega t - \theta_2) = I_m \sin(\omega t - \theta_2 + 90^\circ)$$

$$\text{相位差為: } (\theta_1) - (-\theta_2 + 90^\circ) = \theta_1 + \theta_2 - 90^\circ$$

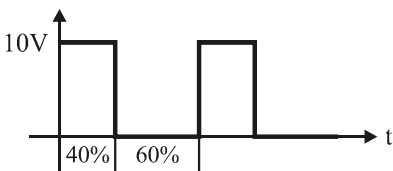44. 波形輸出如下圖所示

$$V_{rms} = \sqrt{\frac{10^2 \times 0.4 + 0^2 \times 0.6}{1}} = \sqrt{40} V$$



45.  $\bar{V}_T = 600 \angle 90^\circ - 600 \angle 30^\circ$   
 $= 600 \angle 90^\circ + 600 \angle 210^\circ = 600 \angle 150^\circ V$

$$\bar{Z} = 40 - j30 = 50 \angle -37^\circ \Omega$$

$$\bar{I} = \frac{\bar{V}_T}{\bar{Z}} = \frac{600 \angle 150^\circ}{50 \angle -37^\circ} = 12 \angle 187^\circ A$$

46. 開關未閉合前, 電路功率因數  $PF = 0.6 = \frac{R}{Z} = \frac{12}{Z}$

$$\therefore Z = 20 = 12 - jX_C , X_C = -j16 \Omega$$

開關閉合後, 電路功率因數  $PF = 0.6$

$$\therefore X_C // X_L = j16 \Omega , \frac{16X_L}{-j16 + jX_L} = j16$$

$$X_L = 16 - X_L \quad \therefore X_L = 8 \Omega$$

47.  $\bar{X}_L = j\omega L = j1 \Omega ; \bar{X}_C = -j \frac{1}{\omega C} = -j1 \Omega$

$$Z = (1 // j1) + (-j1) = \frac{j1}{1 + j1} - j1 = \frac{1}{2} - j \frac{1}{2} \Omega$$

48.  $\bar{Z} = \frac{\bar{E}}{\bar{I}} = \frac{100 \angle 30^\circ}{5 \angle -7^\circ} = 20 \angle 37^\circ = 16 + j12 \Omega$  (串聯)

將  $16 + j12$  化為並聯等效,  $R = \frac{16^2 + 12^2}{16} = 25 \Omega$

49.  $i(t) = 5 \sin(314t)$

$$v(t) = -40 \cos(314t + 30^\circ) = 40 \cos(314t - 150^\circ) = 40 \sin(314t - 60^\circ)$$

$i(t)$  超前  $v(t)$ , 電路呈電容性

$$\omega = 314 \text{ rad/sec} , f_v = f_i = 50 \text{ Hz} , f_p = 100 \text{ Hz}$$

$$\bar{I} = 2.5\sqrt{2} \angle 0^\circ A , \bar{V} = 20\sqrt{2} \angle -60^\circ V$$

$$P = IV \cos \theta = 50 W , S = IV = 100 VA$$

$$P_{MAX} = P + S = 150 W$$

50.  $S = 500\sqrt{2} VA$  ,  $PF = 0.707$  (落後)

$$\therefore Q_C = 500 VAR , Q_C = 500 = \frac{V^2}{X_C} = \frac{(50\sqrt{2})^2}{X_C}$$

$$X_C = \frac{(50\sqrt{2})^2}{500} = 10 \Omega , X_C = \frac{1}{\omega C}$$

$$\therefore C = \frac{1}{\omega X_C} = \frac{1}{5000 \times 10} = 20 \mu F$$